

# Comparator

Vivek Porush

Implementation of Comparator using Op-Amp (LM741)

# **Comparator**

## **Documentation And Reference**


**Analog and Mixed Signal VLSI Design**

**Porush, Vivek**

**[vivek.91.porush@gmail.com](mailto:vivek.91.porush@gmail.com)**

**Aim:** The primary purpose of this project is to design a comparator circuit using *Op-Amp* in SPICE. *SPICE* is industry standard software to design and simulate electrical circuits. It is derived from original SPICE program where, SPICE is acronym for *Simulation Program with Integrated Circuit Emphasis*.

**Design Parameters:** This project deals with implementation of *Op-Amp* as a comparator. As specified by the circuit we have following parameters available:

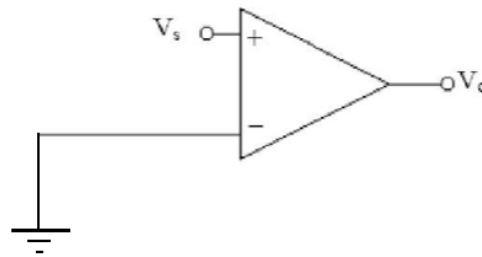

*Figure 1. Circuit implementation of Op- Amp as Comparator & Ground as reference*

Circuit parameters are as follows:

Parameter	Value	Unit	Specification
$V_s$	2.5 @ 1KHZ	V	AC SIN Input Voltage
<i>Op- Amp Biasing Parameters</i>			
Parameter	Value	Unit	Specification
LM741	-	-	Sub circuit from National Semiconductors
$V_{cc} (V+)$	12	V	Positive Bias Voltage
$V_{ee} (V-)$	-12	V	Negative Bias Voltage

*Table 1. Circuit Parameters*

**Required Output:** We are required to observe and verify that the output is a square wave. Moreover we have to observe difference in period if any.

**Theoretical Analysis:** A comparator is a simple circuit that compares two input signals and outputs a discrete signal indicating which one of them is larger. Comparators use the high open loop-gain property of *Op- Amps* and thus are extremely sensitive to small variation in input voltage. Generally reference signal is supplied on one of the inputs of *Op- Amps* and the other input signal is compared to it. Output signal is in accordance with the input terminal (inverting or non-inverting).

In the given design problem  $V_{ref}$  is taken as ground. Thus for all the values of input signal that are greater than  $V_{ref}$  the output will be  $V+$  (open loop gain  $\approx \infty$ ). When input signal drops below the  $V_{ref}$  output signal will also drop to  $V-$ . Thus resulting in a square wave. For a periodic signal the input and output period should be same as output closely follows variation in input signal.

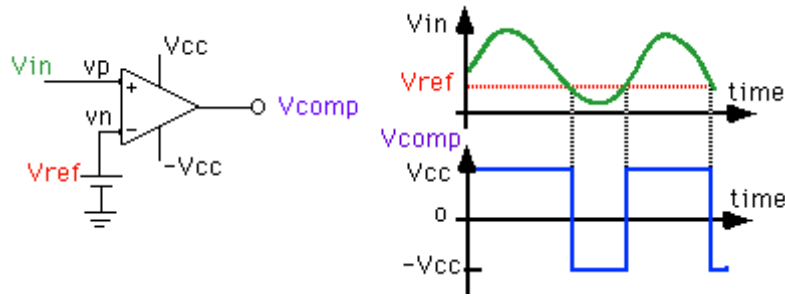


Figure 2. Theoretically anticipated output

**Theoretically anticipated values:** Ideally the output from comparator is  $V_{cc}$  &  $V_{ee}$  for any input voltage greater or smaller than  $V_{ref}$ . However, due to offset voltage, current and other non-ideal effects the output voltage will be smaller. We will call this error and attribute it to non-ideal behavior of Op- Amp.

Voltage Source	$V_s$ Input Voltage	$V_o$ Output Voltage	Unit
$V_s$ (AC)	$0 < V_s \leq 2.5$	+12	V
	$-2.5 \leq V_s < 0$	-12	V

Table 2. Theoretically anticipated output voltages

**Nodal Circuit Diagrams:** The circuit shown below is the nodal (representing ‘nets’) circuit as implemented in the SPICE.

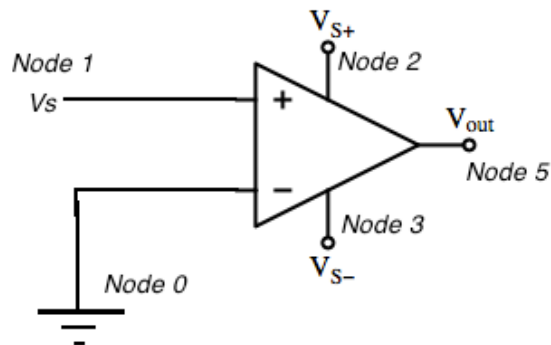


Figure 3. Comparator as implemented in HSPICE

**Error:** Table below shows the error in the output voltage as compared to the theoretical predictions:

Frequency	Input Voltage	Predicted Output Voltage (Peak)	Actual Output Voltage (Peak)	Error (V Peak)
2.5V @1KHz AC	2.5	12	11.023	$0.977 \approx 1$
	-2.5	-12	-11.029	$-0.971 \approx -1$

Table 3. Deviations of  $V_s$  from predicted values

It is clear from the above data that the observed error is  $\pm 1$  V and can attribute it to non-ideal behavior (saturation) of Op- *Amp*.

**Conclusion:** The circuit for Comparator was designed and simulated in *HSPICE* successfully. Following conclusions can be drawn from simulation:

- The observed error is small and can attribute it to non-ideal behavior of Op- *Amp*.
- The output signal is a square wave as expected.
- Period of output signal is same as input signal.

